

P1 Par diferencial CMOS de canal N.

$$V_{CC} = 10V$$

$$V_{EE} = -10V$$

$$V_{GSQ3} = \frac{V_{CC} - V_{EE}}{R_3 + R_4} \cdot R_4 = \frac{10 - (-10)}{440 + 82} \cdot 82 = 3.142V$$

$$I_{DQ3} = K (V_{GSQ3} - V_{TO})^2$$

$$K_P = 0.1 \cdot 10^{-3} \quad L = 0.35 \mu m$$

$$V_{TO} = 0.5 \quad W = 0.5 \mu m$$

$$K = \frac{W}{L} \cdot \frac{K_P}{2} = \frac{0.5}{0.35} \cdot \frac{0.1 \cdot 10^{-3}}{2} = 0.071 \cdot 10^{-3}$$

$$V_{TO} = 0.5$$

$$I_{DQ3} = 0.071 \cdot 10^{-3} \cdot (3.142 - 0.5)^2 = 0.495 \cdot 10^{-3} A$$

$$I_{DQ1,2} = I_{DQ3} / 2 = 248 \mu A$$


$$g_m = 2 \sqrt{K \cdot I_{DQ}} \Rightarrow g_{m1,2} = 2 \sqrt{0.071 \cdot 10^{-3} \cdot 248 \cdot 10^{-6}}$$

$$g_{m1,2} = 0.265 \cdot 10^{-3} S$$

$$V_P = V_{GSQ1,2} = \sqrt{\frac{I_{DQ1,2}}{K}} + V_{TO} = -2.37V$$

$$V_{DQ1,2} = V_{CC} - I_{DQ1,2} \cdot R_{D1,2} = 10 - 248 \cdot 10^{-6} \cdot 20 \cdot 10^3$$

$$V_{DQ1,2} = 5.04V$$

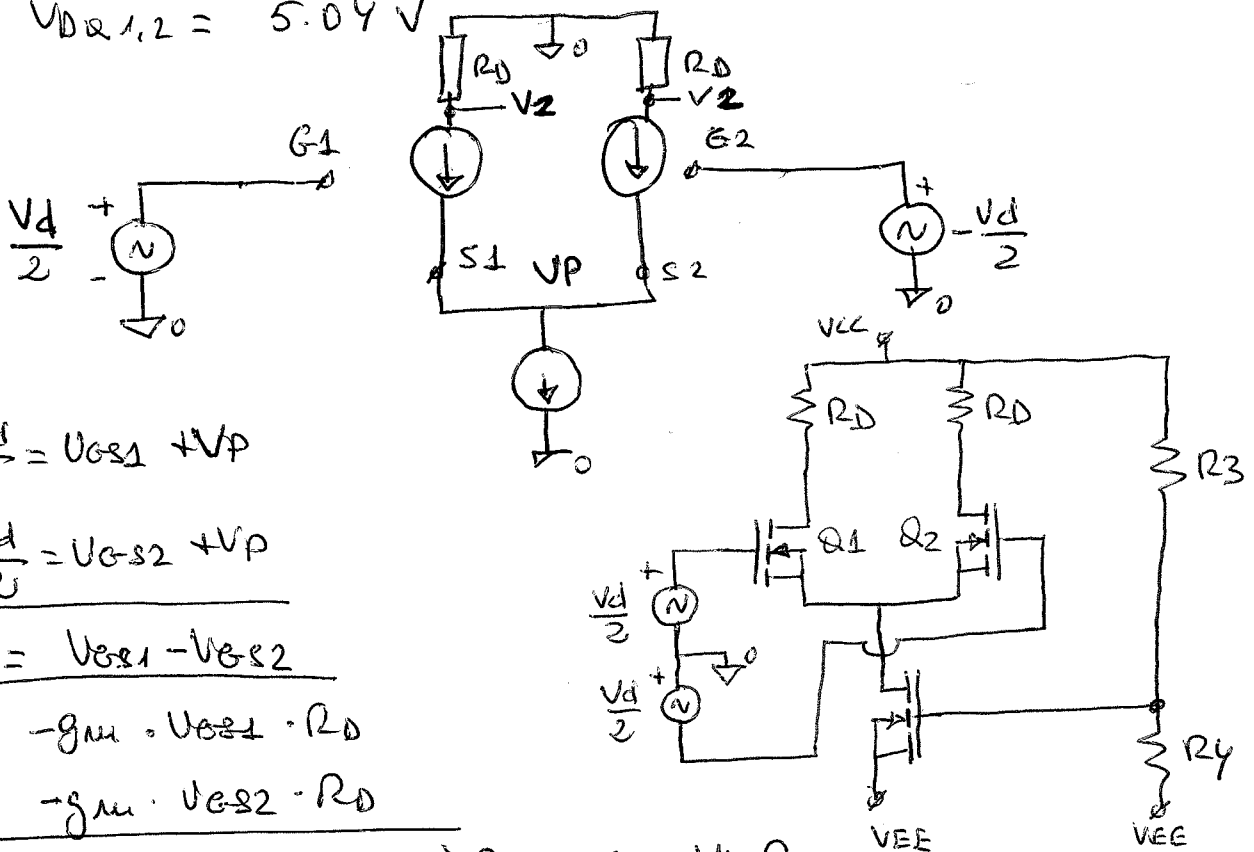

$$\frac{V_d}{2} = V_{GS1} + V_P$$

$$-\frac{V_d}{2} = V_{GS2} + V_P$$

$$V_d = V_{GS1} - V_{GS2}$$



$$V_2 = -g_m \cdot V_{GS1} \cdot R_D$$

$$V_1 = -g_m \cdot V_{GS2} \cdot R_D$$


$$V_2 - V_1 = -g_m (V_{GS1} - V_{GS2}) R_D = -g_m \cdot V_d \cdot R_D$$

$$A_d = -\frac{V_2 - V_1}{V_d} = +g_m \cdot R_D = 5.3$$

(P2) Calcular la ganancia de tensión

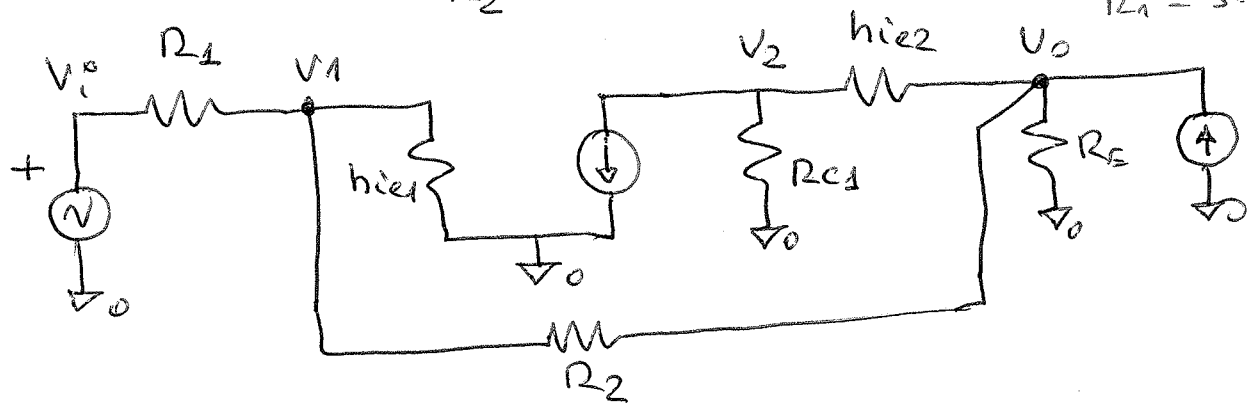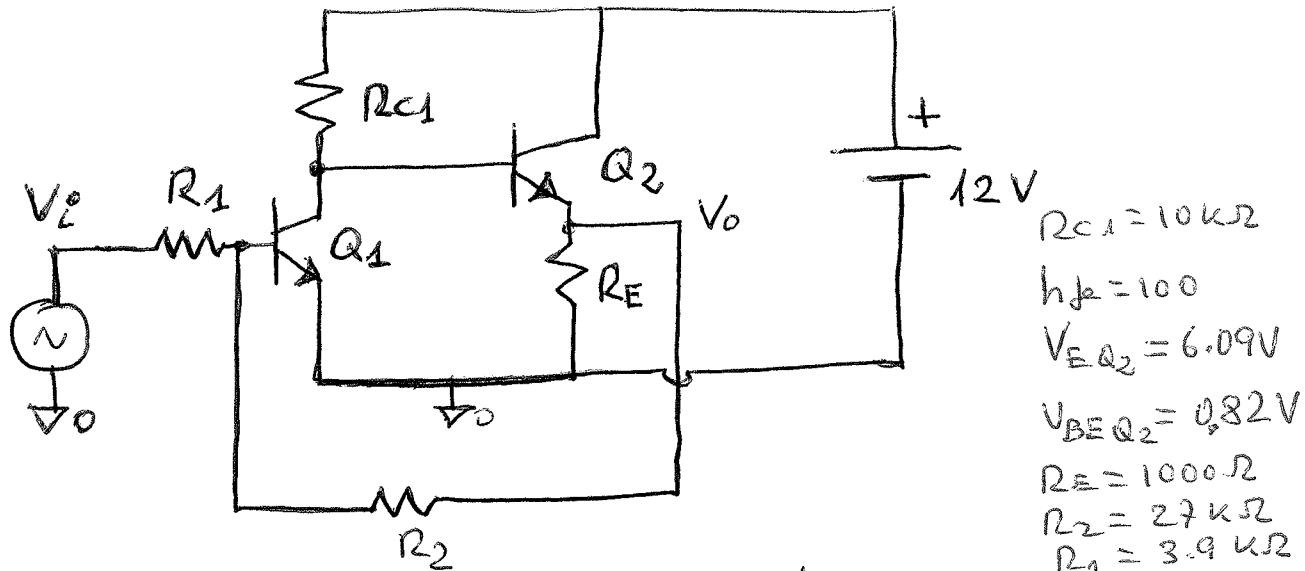

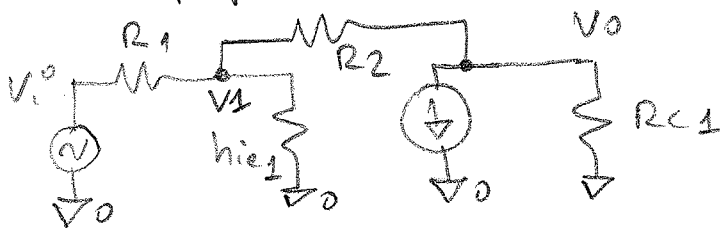- Suponiendo que $V_2 \approx V_o$, ya que Q_2 es un amplificador seguidor de emisor o colector común




$$\begin{aligned} \textcircled{1} \quad \frac{V_1 - V_o}{R_2} &= \frac{V_1}{h_{ie1}} \cdot h_{fe} + \frac{V_o}{R_{c1}} \\ \textcircled{2} \quad \frac{V_i - V_1}{R_1} &= \frac{V_1 - V_o}{R_2} + \frac{V_1}{h_{ie1}} \end{aligned} \quad \left\{ \begin{aligned} \textcircled{1} \quad V_1 \left(1 - \frac{h_{fe} \cdot R_2}{h_{ie1}} \right) &= V_o \left(1 + \frac{R_2}{R_{c1}} \right) \\ V_1 \cdot \left(1 - \frac{100 \cdot 27000}{5784} \right) &= V_o \left(1 + \frac{27}{10} \right) \\ V_1 \cdot (-465.8) &= 3.7 \cdot V_o \\ \boxed{V_1} &= -7.94 \cdot 10^{-3} \cdot V_o \end{aligned} \right.$$

$$V_i = -V_o \frac{R_1}{R_2} + V_1 \left(\frac{R_1}{h_{ie1}} + 1 + \frac{R_1}{R_2} \right)$$

$$\boxed{V_i = -0.144 \cdot V_o + V_1 \cdot 1.818}$$

$$V_i = -0.144 V_o + 1.818 \cdot (-7.94 \cdot 10^{-3}) \cdot V_o = -0.158 V_o$$

$$\boxed{A_v = -6.31}$$

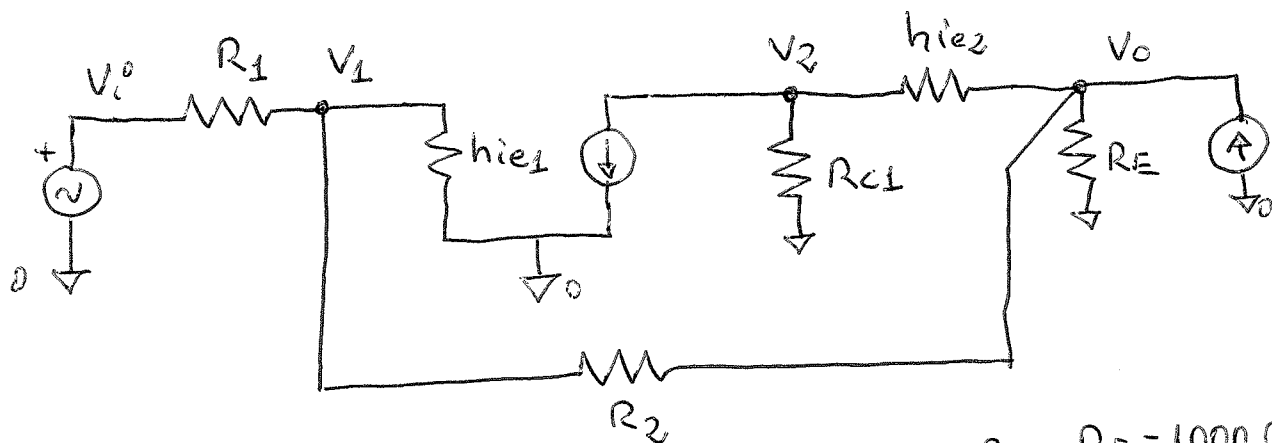

$$R_1 = 3 \text{ k}\Omega ; R_2 = 27 \text{ k}\Omega ; R_{c1} = 10 \text{ k}\Omega ; R_E = 1000 \Omega$$

$$V_{EQ2} = 6.09 \text{ V} ; h_{fe_{Q1, Q2}} = 100$$

$$\textcircled{1} \quad \frac{V_1}{h_{ie1}} = \frac{V_i - V_1}{R_1} + \frac{V_2 - V_1}{R_2} \Rightarrow V_1 \left(\frac{1}{h_{ie1}} + \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_i}{R_1} + \frac{V_2}{R_2}$$

$$V_1 \left(\frac{R_1 + R_2 + h_{ie1}}{h_{ie1}} \right) = V_i \cdot R_2 + V_2 \cdot R_1$$

$$V_1 = 4.257 V_i + 6.15 V_2$$

$$\textcircled{2} \quad \frac{V_2}{R_{c1}} + \frac{V_1}{h_{ie1}} \cdot h_{fe} + \frac{V_2 - V_o}{h_{ie2}} = 0 \Rightarrow V_2 \left(\frac{1}{R_{c1}} + \frac{1}{h_{ie2}} \right) + V_1 \cdot \frac{h_{fe}}{h_{ie1}} = \frac{V_o}{h_{ie2}}$$

$$\Rightarrow V_2 \cdot \frac{R_{c1} + h_{ie2}}{R_{c1}} + V_1 \cdot \frac{h_{fe} \cdot h_{ie2}}{h_{ie1}} = V_o$$

$$1041 \cdot V_2 + 7.088 V_1 = V_o$$

$$V_2 = 0.96 V_o - 6.8 \cdot V_1$$

$$\textcircled{3} \quad \frac{V_2 - V_o}{h_{ie2}} (1 + h_{fe}) = \frac{V_o}{R_E} + \frac{V_o - V_1}{R_2}$$

$$V_2 \cdot \frac{1 + h_{fe}}{h_{ie2}} - V_o \cdot \frac{1 + h_{fe}}{h_{ie2}} = V_o \cdot \frac{1}{R_E} + V_o \cdot \frac{1}{R_2} - V_1 \cdot \frac{1}{R_2}$$

$$V_2 = \frac{h_{ie2}}{1 + h_{fe}} \left[V_o \left(\frac{1 + h_{fe}}{h_{ie2}} + \frac{1}{R_E} + \frac{1}{R_2} \right) - \frac{V_1}{R_2} \right]$$

$$V_2 = 4.059 \cdot [V_o \cdot 0.256 - V_1 \cdot 3.7037 \cdot 10^{-5}]$$

$$V_2 = 1.041 \cdot V_o - 1.5 \cdot 10^{-4} V_1$$

$$0.96 V_o - 6.8 \cdot (4.257 V_i + 6.15 V_o) = 1.041 \cdot V_o - 1.5 \cdot 10^{-4} \cdot (4.257 V_i + 6.15 V_o)$$

$$V_o (0.96 - 4182 - 1.041 + 0.092) = (28947 - 0.638) V_i$$

$$A_v = -6.9$$

$$h_{ie1} = \frac{100 \cdot 25.8}{0.446} = 5784 \Omega ; h_{ie2} = \frac{100 \cdot 25.8}{6.287} = 410 \Omega$$