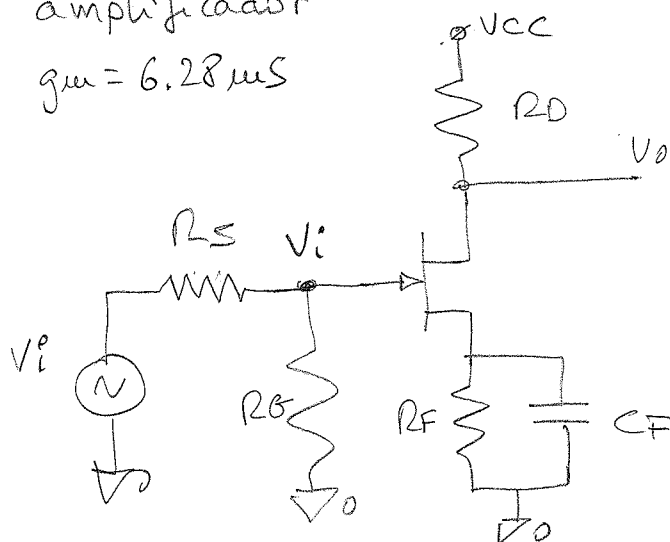


① Calcular la respuesta en frecuencia del siguiente amplificador

$$g_m = 6.28 \text{ mS}$$



$$R_D = 5 \text{ k}\Omega$$

$$C_{gd} = 4.57 \text{ pF}$$

$$C_{gs} = 4.06 \text{ pF}$$

$$R_F = 1000 \Omega$$


$$C_G = C_{gs} + C_{gd}(1 - K)$$

$$C_G = 4.06 + 4.57(1 - (-31.4))$$

$$C_G = 152.128 \text{ pF}$$

$$C_D = C_{gd} \left(1 - \frac{1}{K}\right) = 4.71 \text{ pF}$$

altas frecuencias:

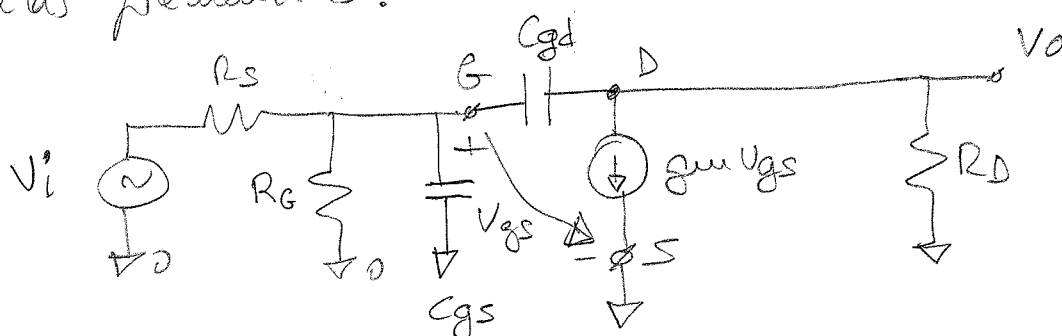

A_v (frecuencias medias) $\Rightarrow V_g = V_i \cdot \frac{R_G}{R_G + R_S} = V_{gs}$

$$A_v = -6.28 \cdot 10^{-3} \cdot \frac{2 \cdot 10^6}{2 \cdot 10^6 + 50} \cdot 5 \cdot 10^3$$



$$V_O = -g_m \frac{R_G}{R_G + R_S} \cdot R_D \cdot V_i$$

$$A_v = -31.4 \Rightarrow 20 \log A_v = 29.93 \text{ dB}$$

$\Rightarrow$ Miller

$$K = -R_D \cdot g_m = \frac{V_O}{V_G}$$

$$= -31.4$$

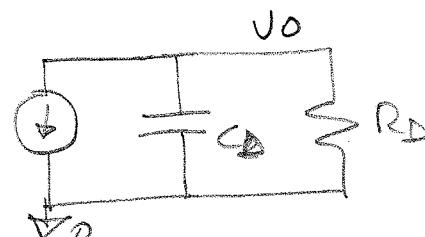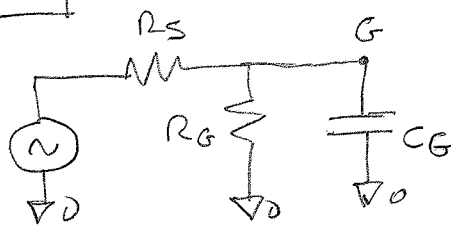


$$P_1 \Rightarrow f_{P1} = \frac{1}{2\pi (R_S // R_G) \cdot C_G} = \frac{1}{2\pi \cdot 49.98 \cdot 152.128 \cdot 10^{-12}}$$

$$f_{P1} = 20.93 \text{ MHz}$$

$$P_2 \Rightarrow f_{P2} = \frac{1}{2\pi R_D C_D} = \frac{1}{2\pi \cdot 5.000 \cdot 4.71 \cdot 10^{-12}} = 6.75 \text{ MHz}$$

$$f_{P2} = 7.2 \text{ MHz}$$

A frecuencia cero

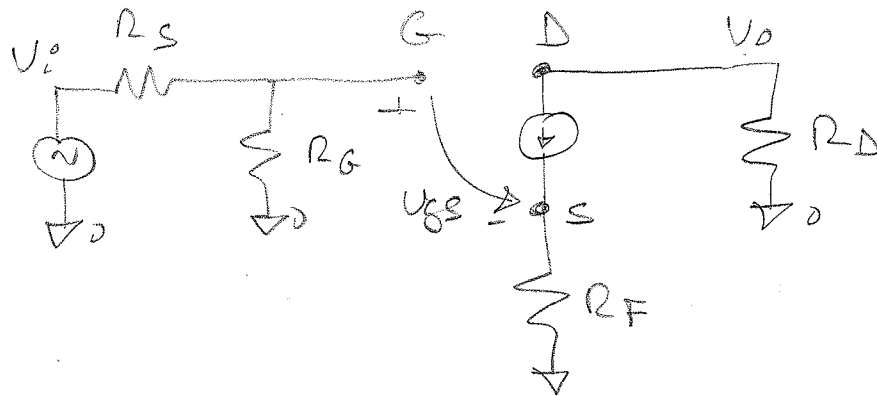

$$V_E = g_m \cdot V_{GS} \cdot R_F$$

$$V_G = V_i \cdot \frac{R_G}{R_S + R_G}$$

$$V_{GS} = V_i \cdot \frac{R_G}{R_S + R_G} - g_m V_{GS} R_F$$

$$V_{GS} (1 + g_m R_F) = V_i \cdot \frac{R_G}{R_S + R_G}$$

$$V_o = -g_m \cdot R_D \cdot V_i \cdot \frac{R_G}{(R_S + R_G)(1 + g_m R_F)}$$

$$A_v(f=0) = \frac{-g_m \cdot R_D \cdot R_G}{(R_S + R_G)(1 + g_m R_F)}$$

$$A_v(f=0) = \frac{-6.28 \cdot 10^{-3} \cdot 5000 \cdot 2 \cdot 10^6}{(50 + 2 \cdot 10^6)(1 + 6.28 \cdot 10^{-3} \cdot 1000)} = -4.31$$

$$\downarrow$$

$$12.69 \text{ dB}$$

A baja frecuencia

$$R_F // C_F = \frac{R_F \cdot \frac{-j}{\omega C_F}}{R_F - \frac{j}{\omega C_F}} =$$

$$= \frac{-j R_F}{\omega C_F R_F - j} = \frac{R_F}{j \omega C_F R_F + 1} \Rightarrow Z_F = \frac{R_F}{s \cdot C_F R_F + 1}$$


$$\Rightarrow 1 + g_m \cdot Z_F = 1 + g_m \cdot \frac{R_F}{s \cdot C_F R_F + 1} = \frac{s \cdot C_F R_F + 1 + g_m R_F}{s \cdot C_F R_F + 1}$$

$$\Rightarrow A_v(\text{baja } f) = \frac{-g_m \cdot R_D \cdot R_G}{(R_S + R_G) \cdot (1 + g_m R_F)} \cdot \frac{s \cdot C_F R_F + 1}{s \cdot \frac{C_F R_F}{1 + g_m R_F} + 1}$$


$$\text{Zero en } Z_1 = \frac{1}{2\pi R_F C_F} = \frac{1}{2\pi \cdot 1000 \cdot 50 \cdot 10^{-6}} = 3.18 \text{ Hz} = Z_1$$

$$\text{polo en } p_3 = \frac{1 + g_m \cdot R_F}{2\pi C_F R_F} = 22.92 \text{ Hz} = p_3$$

Diagrama de Bode

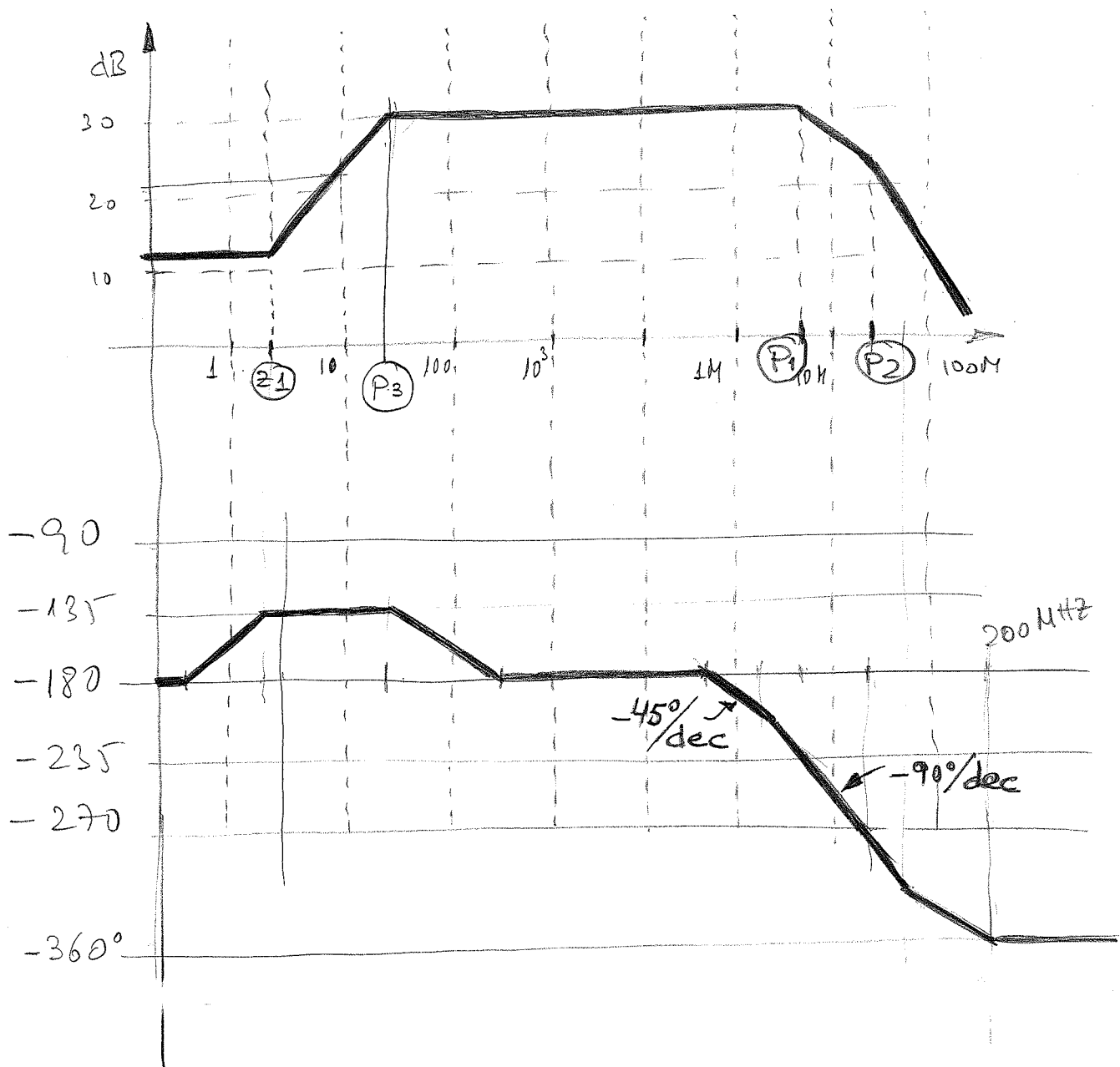

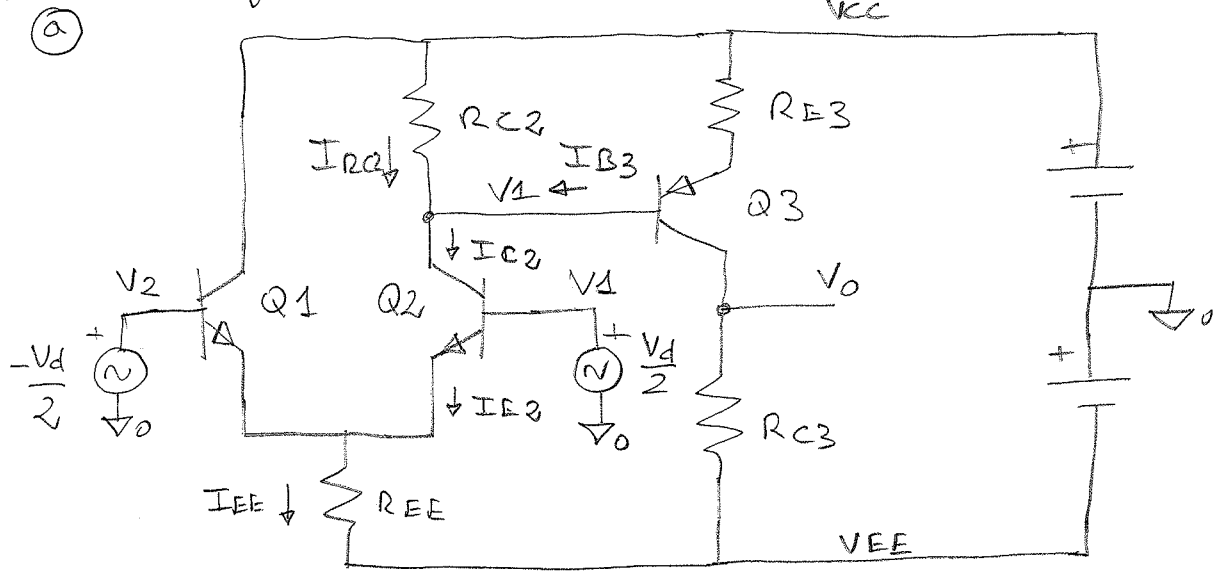② En el siguiente circuito calcular R_{C2} y R_{E3} .



$$\beta = 100, R_{EE} = 10\text{ k}\Omega, R_{E3} = 2\text{ k}\Omega$$

$$V_{CC} = 12\text{ V}, V_{EE} = -12\text{ V}, V_O = 0\text{ V}, V_1 = 9\text{ V}$$

$$V_{BE Q2} = 0.76\text{ V}, V_{BE Q3} = 0.82\text{ V}$$

$$① I_{E2} = \frac{1}{2} I_{EE} = \frac{1}{2} \frac{|V_{EE}| - V_{BE Q2}}{R_{EE}} = \frac{1}{2} \frac{12 - 0.76}{10\text{ k}\Omega} = 562\text{ }\mu\text{A}$$

$$② I_{C2} = I_{E2} \cdot \frac{\beta}{1 + \beta} = 556.4\text{ }\mu\text{A}$$

$$③ \frac{V_O - V_{EE}}{R_{C3}} = I_{C3} = \frac{0 - (-12)}{2\text{ k}\Omega} = 6\text{ mA}$$

$$I_{B3} = \frac{I_{C3}}{\beta} = 0.06\text{ mA} = 60\text{ }\mu\text{A}$$


$$④ \frac{V_{CC} - V_{BE Q3} - V_1}{R_{E3}} = I_{E3} = I_{B3} + I_{C3} = 6.06\text{ mA}$$

$$R_{E3} = \frac{12 - 0.82 - 9}{6.06\text{ mA}} = 360\text{ }\Omega$$

$$⑤ I_{RC2} = I_{C2} - I_{B3} = 556.4\text{ }\mu\text{A} - 60\text{ }\mu\text{A} = 496.4\text{ }\mu\text{A}$$

$$R_{C2} = \frac{V_{CC} - V_1}{I_{RC2}} = 6043\text{ }\Omega$$

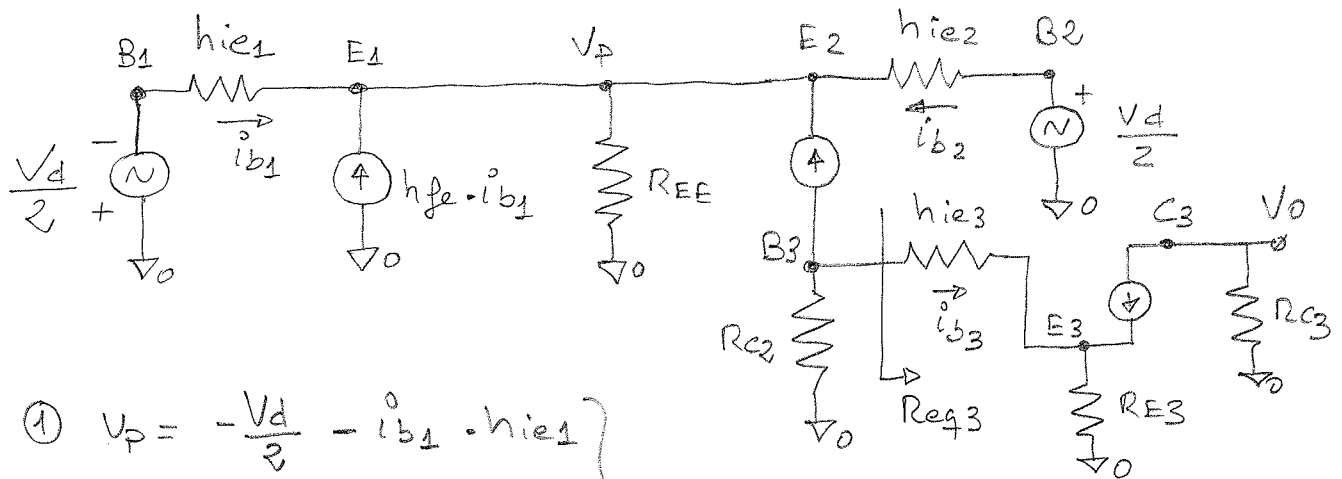(2) b) Calcular la ganancia: $A_V = \frac{V_o}{V_1 - V_2} = \frac{V_o}{V_d}$



$$(1) V_p = -\frac{V_d}{2} - i_{b1} \cdot h_{ie1}$$

$$(2) V_p = \frac{V_d}{2} - i_{b2} \cdot h_{ie2} \Rightarrow 2V_p = -(i_{b1} + i_{b2}) \cdot h_{ie} \quad (3)$$

$$(4) (i_{b1} + i_{b2}) \cdot (1 + h_{fe}) = \frac{V_p}{R_{EE}} \xRightarrow{(3)} 2V_p = \frac{-V_p}{(1 + h_{fe}) R_{EE}} \cdot h_{ie} \Rightarrow \boxed{V_p = 0}$$

$$(5) \text{ como } V_p = 0 \Rightarrow i_{b2} = \frac{V_d}{2 h_{ie2}}$$

$$(6) i_{c2} = i_{b2} \cdot h_{fe} = \frac{V_d}{2 h_{ie2}} \cdot h_{fe}$$

$$(7) V_{B3} = -i_{c2} \cdot (R_{C2} \parallel R_{eq3}) \stackrel{(6)}{=} -\frac{V_d \cdot h_{fe}}{2 h_{ie2}} \cdot \frac{R_{C2} \cdot [h_{ie3} + R_{E3}(1 + h_{fe})]}{R_{C2} + h_{ie3} + R_{E3}(1 + h_{fe})}$$

$$(8) A_{V1} = \frac{V_{B3}}{V_d} = -\frac{100}{2 \cdot 4607} \cdot \frac{6043 \cdot [430 + 360 \cdot 101]}{6043 + 430 + 360 \cdot 101} = -56.3$$

$$h_{ie2} = \frac{h_{fe} \cdot V_T}{I_{C2Q}} = \frac{100 \cdot 25.8}{0.56} = 4607 \Omega$$

$$h_{ie3} = \frac{h_{fe} \cdot V_T}{I_{C3Q}} = \frac{100 \cdot 25.8}{6} = 430 \Omega$$

$$(9) A_{V2} = \frac{V_o}{V_{B3}} = \frac{-R_{C3} \cdot h_{fe} \cdot i_{b3}}{i_{b3} \cdot h_{ie3} + i_{b3} (1 + h_{fe}) \cdot R_{E3}} = \frac{-2000 \cdot 100}{430 + 101 \cdot 360}$$

$$A_{V2} = -5.44 \Rightarrow \boxed{A_d = A_{V1} \cdot A_{V2} = 306.27}$$